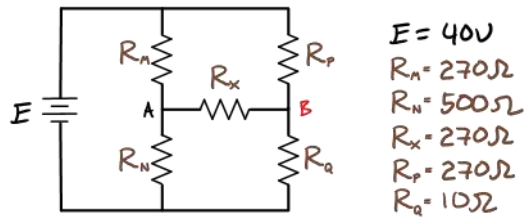


Complex DC Circuit Analysis

Use a delta to y conversion to determine the voltage across the bridge element R_x .



Use Thevenin's Theorem to determine the voltage across the bridge element R_x .

