

### Parallel DC Circuits Examples: Level 1 (11:44)


Determine the voltage drop across each element, the current through each element, the power consumed by each element, source current, and total power.



Determine the voltage drop across each element, the current through each element, the power consumed by each element, source current, and total power.



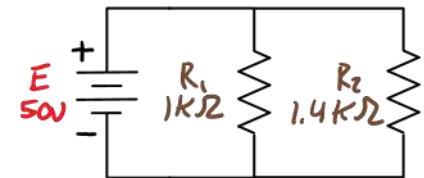determine the voltage drop across each element, the current through each element, the power consumed by each element, source current, and total power.



Determine the voltage drop across each element, the current through each element, the power consumed by each element, source current, and total power.



Determine the voltage drop across each element, the current through each element, and source current.

