
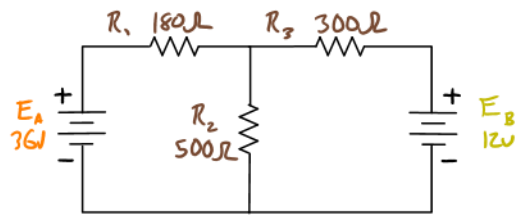


DC Superposition Theorem Examples

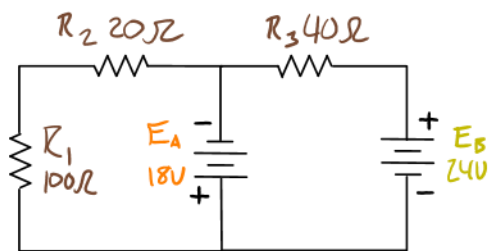
Use the superposition theorem to determine electrical properties of this circuit.



Use the superposition theorem to determine electrical properties of this circuit.



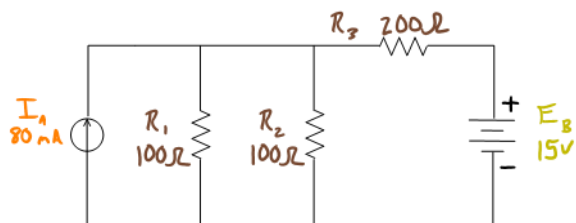Use the superposition theorem to determine electrical properties of this circuit.



Use the superposition theorem to determine electrical properties of this circuit.

