

### AC Ohms Law Examples (38:03)

Given the following information solve for the desired property. Draw phasors on a phasor diagram.

<p>① <math>\bar{V} = 24V \angle 0^\circ</math>  <math>\bar{Z} = 120\Omega \angle 45^\circ</math>  <math>\bar{I} =</math></p>	<p>② <math>\bar{I} = 400mA \angle 0^\circ</math>  <math>\bar{Z} = 150\Omega \angle 0^\circ</math>  <math>\bar{V} =</math></p>	<p>③ <math>\bar{V} = 32V \angle 0^\circ</math>  <math>\bar{I} = 80mA \angle 45^\circ</math>  <math>\bar{Z} =</math></p>
--	---	---

Determine the relative phase shift of current with respect to voltage for the previous set of example problems.

Given the following information solve for the desired property. Draw phasors on a phasor diagram.

<p>① <math>\bar{I} = 120mA \angle 25^\circ</math>  <math>\bar{Z} = 240\Omega \angle 10^\circ</math>  <math>\bar{V} =</math></p>	<p>② <math>\bar{V} = 56V \angle 30^\circ</math>  <math>\bar{I} = 180mA \angle 120^\circ</math>  <math>\bar{Z} =</math></p>	<p>③ <math>\bar{V} = 80V \angle 90^\circ</math>  <math>\bar{Z} = 400\Omega \angle 90^\circ</math>  <math>\bar{I} =</math></p>
---	--	---


Determine the relative phase shift of current with respect to voltage for the previous set of example problems.

Given the following information solve for the desired property. Draw phasors on a phasor diagram.


<p>① <math>\bar{V} = 120V \angle 0^\circ</math>  <math>\bar{I} = 1.3A \angle 30^\circ</math>  <math>\bar{Z} =</math></p>	<p>② <math>\bar{V} = 96V \angle 20^\circ</math>  <math>\bar{Z} = 190\Omega \angle -35^\circ</math>  <math>\bar{I} =</math></p>	<p>③ <math>\bar{I} = 86mA \angle -10^\circ</math>  <math>\bar{Z} = 200\Omega \angle 50^\circ</math>  <math>\bar{V} =</math></p>
--	--	---

Determine the relative phase shift of current with respect to voltage for the previous set of example problems.

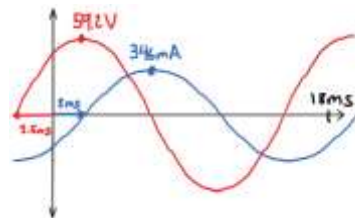
Given the following information solve for the impedance. Draw phasors on a phasor diagram. Determine the relative phase shift of current with respect to voltage.



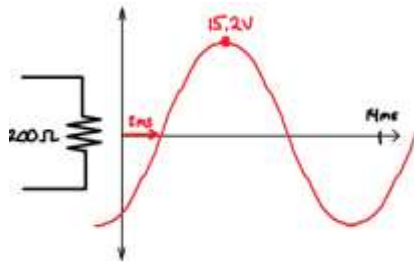
Given the following information solve for current. Draw phasors on a phasor diagram. Determine the relative phase shift of current with respect to voltage.



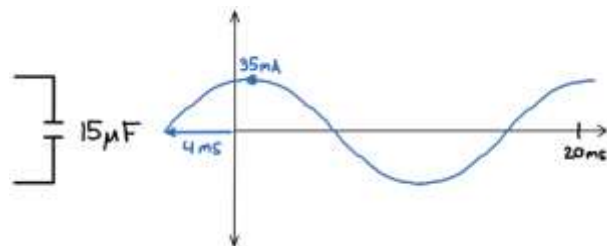Given the following information solve for voltage. Draw phasors on a phasor diagram. Determine the relative phase shift of current with respect to voltage.



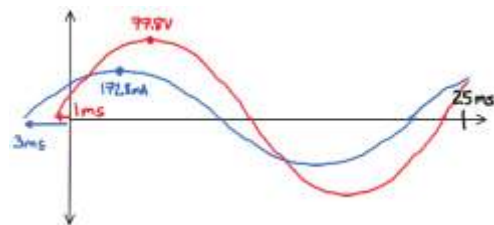Given the following information solve for the impedance and the components that comprise this impedance. Draw phasors on a phasor diagram. Determine the relative phase shift of current with respect to voltage.



Given the coil of a contactor modeled as:

- 1) a  $10\ \Omega$  resistance in series with a  $10\text{mH}$  inductor when initially energized and the contact carrier is not pulled into the coil
  - 2) a  $10\ \Omega$  resistance in series with a  $1.5\text{H}$  inductor when the contact carrier is fully pulled into the coil
- Explain why the coil burns out if the coil is energized by  $120\text{V}$ ,  $60\text{Hz}$  AC but an obstruction prevents the plunger from being pulled into the coil.

Explain why the above coil, rated for  $120\text{V}$ ,  $60\text{Hz}$  AC, burns out when energized by  $24\text{V}$  DC.

Explain why motor drives commonly use  $\text{V}/\text{Hz}$  control where, as frequency is increased, voltage is also increased. As a practical example, consider a motor winding modeled as a  $110$  resistor in series with a  $170\text{mH}$  inductor. Assume the motor enters overload conditions if current is above  $1.75\text{A}$ . Consider two operating points:  $208\text{V}$  at  $60\text{Hz}$  and  $104\text{V}$  at  $30\text{Hz}$