

AC Superposition Theorem (20:27)

Describe the superposition theorem in general terms.

Describe the disadvantages and limitations of the superposition theorem.

List the methods of removing voltage and current sources from consideration.

List the steps of the superposition theorem.

Apply the superposition theorem to solve for electrical properties of elements in this circuit.

