

Delta Configurations (38:31)


Given a 3 phase AC system with 120V line to neutral differentials phase shifted from each other by a relative 120°, determine the line to line differentials assuming L1 to neutral is the reference. Draw this on a phasor diagram. Determine the same phasor equivalents when L1-L2 is assumed to be the reference. Draw this on a phasor diagram.

Draw a delta configured load. Identify which voltage loads in a delta configuration experience.

Identify how current flows through the lines and loads in a delta configuration. Draw a diagram.

Summarize the electrical characteristics of delta configured loads.

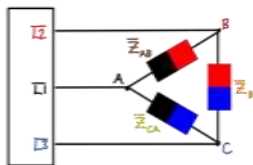Given this balanced delta configured load determine the voltage, current, and power for each load, line current, and total power.



$$Z_{AB} = 400 \Omega \angle 20^\circ$$

$$Z_{BC} = 400 \Omega \angle 20^\circ$$

$$Z_{CA} = 400 \Omega \angle 20^\circ$$

$$\text{REF: } I_1 - I_2 = 208V \angle 0^\circ = \bar{V}_{AB}$$


$$I_2 - I_3 = 208V \angle -120^\circ = \bar{V}_{BC}$$

$$I_3 - I_1 = 208V \angle 120^\circ = \bar{V}_{CA}$$

Identify a short cut method of determining electrical properties for individual loads and total power in a balanced delta configuration.

Identify a short cut method of determining line current given known load current in a balanced delta configuration.

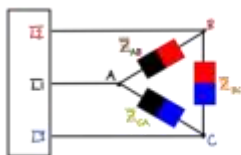Given this unbalanced delta configured load determine the voltage, current, and power for each load, line current, and total power.



$$Z_{AB} = 500 \Omega \angle 90^\circ$$

$$Z_{BC} = 400 \Omega \angle 20^\circ$$


$$Z_{CA} = 400 \Omega \angle 20^\circ$$

$$\text{REF: } I_1 - I_2 = 208V \angle 0^\circ = \bar{V}_{AB}$$

$$I_2 - I_3 = 208V \angle -120^\circ = \bar{V}_{BC}$$


$$I_3 - I_1 = 208V \angle 120^\circ = \bar{V}_{CA}$$

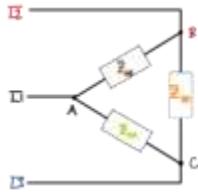Given this balanced delta configured load determine the voltage, current, and power for each load, line current, and total power.



REF: $\vec{V}_{AB} = 480\text{V} \angle 0^\circ = \vec{V}_{AB}$
 $\vec{V}_{BC} = 480\text{V} \angle -120^\circ = \vec{V}_{BC}$
 $\vec{V}_{CA} = 480\text{V} \angle 120^\circ = \vec{V}_{CA}$
 $\vec{Z}_{AB} = 320 \Omega \angle 35^\circ$
 $\vec{Z}_{BC} = 320 \Omega \angle 35^\circ$
 $\vec{Z}_{CA} = 320 \Omega \angle 35^\circ$

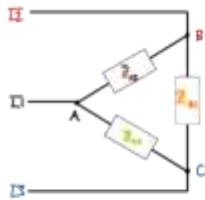Given this unbalanced delta configured load determine the voltage, current, and power for each load, line current, and total power.



REF: $\vec{V}_{AB} = 480\text{V} \angle 0^\circ = \vec{V}_{AB}$
 $\vec{V}_{BC} = 480\text{V} \angle -120^\circ = \vec{V}_{BC}$
 $\vec{V}_{CA} = 480\text{V} \angle 120^\circ = \vec{V}_{CA}$
 $\vec{Z}_{AB} = 320 \Omega \angle 35^\circ$
 $\vec{Z}_{BC} = 200 \Omega \angle 45^\circ$
 $\vec{Z}_{CA} = 320 \Omega \angle 35^\circ$